

Comax_A1_DR2

Q2	Nature du Convertisseur Continu-continu :	
Q3	<p>The diagram illustrates a dual-channel DC-DC converter. It consists of two identical channels, Channel 1 and Channel 2. Each channel includes a CHARGE PUMP, CONTROL LOGIC, GATE DRIVE, and a DMOS Full Bridge. The control logic is fed by VDD, VREF1, VREF2, and feedback signals Sense1 and Sense2. The output of each channel is connected to a load inductor and a sense resistor (Rs1, Rs2).</p>	
Q4	Règles d'association des sources :	
Q5	Composants	Technologie
Q6	Valeurs limites :	
Q7	Excursion de la tension de commande du hacheur	
Q8	Rôle de la résistance Rs	