
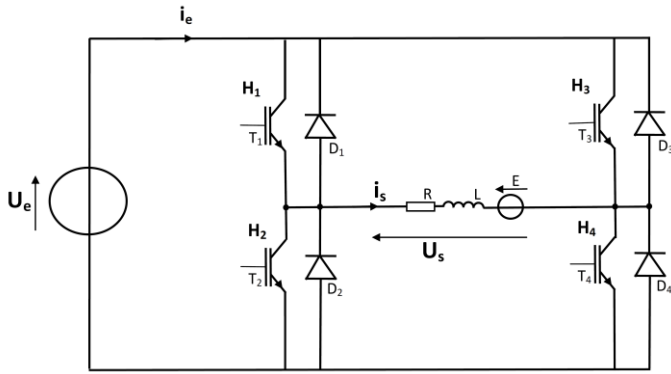


MAXPID_A2_DR1

Q6

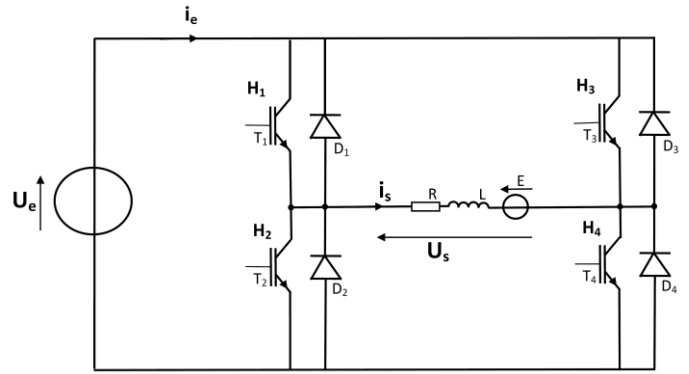


Q7



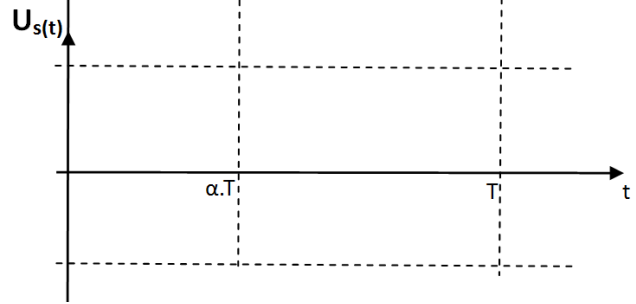Q8


Interrupteurs commandés H₁ et H₄ H₂ et H₃



Q9


Q10

$0 < t < \alpha T$

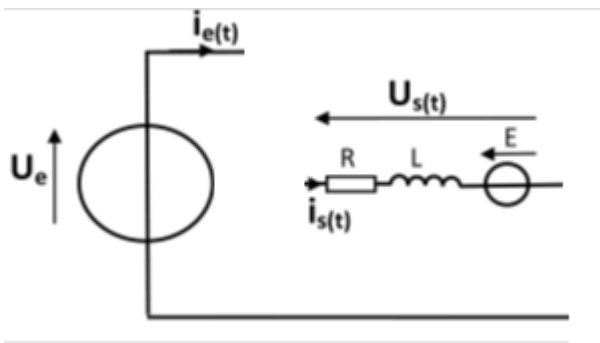

Q11


$\alpha T < t < T$

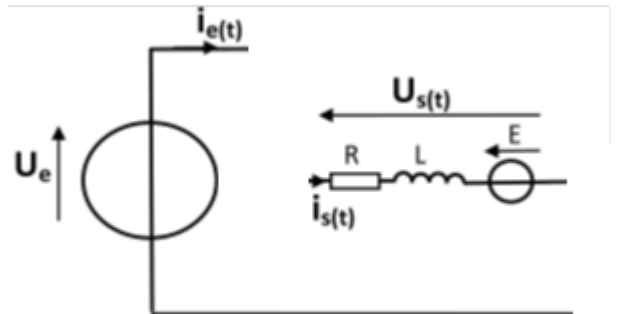


Q12 $0 < t < \alpha.T$

Q13 $\alpha.T < t < T$

Q14 $0 < t < \alpha.T$

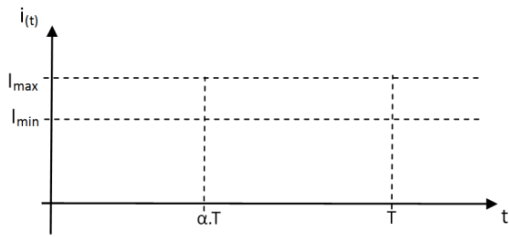

Q15 $\alpha.T < t < T$

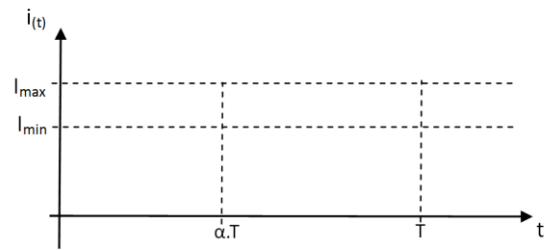

Q16 Calcul de Δi_s

Q17

Q18

Q19

Q20